

(6 pages)

Reg. No. :

**Code No. : 30312 E Sub. Code : JMPH 61/
SMPH 61**

B.Sc. (CBCS) DEGREE EXAMINATION,
APRIL 2020.

Sixth Semester

Physics – Main

DIGITAL ELECTRONICS

(For those who joined in July 2016 onwards)

Time : Three hours

Maximum : 75 marks

PART A — ($10 \times 1 = 10$ marks)

Answer ALL questions.

Choose the correct answer :

1. The number of bits in a binary number of length 2 bytes is _____.
(a) 8 (b) 4
(c) 16 (d) none

2. The one's complement of 10010 is _____.
- (a) 01101 (b) 011100
(c) 11111 (d) none
3. According to De Morgan's first theorem, $\overline{A+B} =$
- (a) $\overline{A \cdot B}$ (b) $\overline{A} + \overline{B}$
(c) $\overline{A} \cdot \overline{B}$ (d) none
4. The OR gate is equivalent to _____ of inputs.
- (a) Product (b) Sum
(c) Subtraction (d) None
5. A flip flop is a bistable electronic device that has _____ stable states.
- (a) three (b) one
(c) two (d) none
6. The condition for carry in a Half Adder is _____.
- (a) $C = A + B$ (b) $C = A - B$
(c) $C = A \cdot B$ (d) none

7. For a n -variable problem there can be _____ minterms.
- (a) $2n$ (b) $2/n$
(c) 2^n (d) none
8. The don't care condition in a Karnaugh map is referred by _____.
- (a) 1 (b) 0
(c) X (d) none
9. Shift Register is used to _____ pulses.
- (a) Add (b) Subtract
(c) Count (d) None
10. The A/D converter, converts _____ in to _____.
- (a) analog, digital (b) digital, analog
(c) decimal, binary (d) none

PART B — ($5 \times 5 = 25$ marks)

Answer ALL questions, choosing either (a) or (b).

Answer should not exceed 250 words.

11. (a) Convert the hexadecimal numbers 2F59 and AB10 into binary numbers.

Or

- (b) Explain the excess three code with an example.

12. (a) State and prove De Morgan's theorems.

Or

- (b) Draw the symbols and truth tables for AND and OR gates.

13. (a) Explain the working of Half adder.

Or

- (b) Explain the working of R-S flip-flop.

14. (a) Explain two variable Karnaugh map.

Or

- (b) Explain the implementation of POS form using NAND gate.

15. (a) What are the types of Registers?

Or

- (b) Explain the working of Asynchronous counter.

PART C — ($5 \times 8 = 40$ marks)

Answer ALL questions, choosing either (a) or (b).

Answer should not exceed 600 words.

16. (a) Explain the conversion of
- (i) hexadecimal number into binary number and
 - (ii) binary number into hexadecimal number.

Or

- (b) Explain binary subtraction by 2's complement method with an example.

17. (a) Explain the postulate and theorems of Boolean algebra.

Or

- (b) Explain the universality of NOR gate.

18. (a) Explain the working of Full adder.

Or

- (b) What are the types of flip-flop? Explain the working of Master Slave flip-flop.

19. (a) Explain the SOP form of Boolean functions.

Or

- (b) Using Karnaugh map simplify :

$$Y = F(A, B, C, D) = \sum M(7, 9, 10, 11, 12, 13, 14, 15)$$

20. (a) Explain the working of decade counter.

Or

- (b) Explain the working of D/A converter.
