

Code No. : 20034 E Sub. Code : SMPH 51

B.Sc. (CBCS) DEGREE EXAMINATION,
NOVEMBER 2022.

Fifth Semester

Physics — Main

BASIC ELECTRONICS

(For those who joined in July 2017–2019)

Time : Three hours

Maximum : 75 marks

PART A — (10 × 1 = 10 marks)

Answer ALL questions.

Choose the correct answer :

1. In Norton's current source
- Short the load resistor
 - Disconnect the load resistor
 - Short the voltage source
 - Open the voltage source

7. The common mode gain is
- very high
 - very low
 - always unity
 - unpredictable
8. In a Colpitt's oscillator, the feedback is obtained
- by magnetic induction
 - by a tickler coil
 - from the center of split capacitors
 - none of these
9. In ideal op - amp the I/P impedance is _____
- infinite
 - zero
 - 1
 - constant
10. The gain of an actual op - amp is around
- 10,00,000
 - 1,000
 - 100
 - 15 V

PART B — (5 × 5 = 25 marks)

Answer ALL questions choosing either (a) or (b).
Each answer should not exceed 250 words.

11. (a) State and Explain Norton's theorem.
- Or
- (b) How will you determine the h-parameters of a linear circuit?

Page 3 Code No. : 20034 E

2. In ideal current source the output current is
- zero
 - constant
 - dependent on load
 - dependent on internal resistance
3. For break down in zener diode the requirement is
- forward bias
 - reverse bias
 - both forward and reverse bias
 - none
4. The ac beta given by $\beta_{ac} = \frac{\Delta I_C}{\Delta I_B}$
- $\Delta I_C / \Delta I_B$
 - $\Delta I_C \times \Delta I_B$
 - $\Delta I_E / \Delta I_B$
 - $\Delta I_E \times \Delta I_B$
5. A MOSFET has _____ terminals.
- two
 - five
 - four
 - three
6. In a P - channel JFET, the charge carriers are
- electrons
 - holes
 - both electrons and holes
 - none of these

Page 2 Code No. : 20034 E

12. (a) Describe the working of P – N junction diode discuss its uses.
- Or
- (b) Define stability factor. Derive an expression for it.
13. (a) Write a note on JFET connections.
- Or
- (b) Explain the operation of JFET as an amplifier.
14. (a) Using a circuit diagram explain the working of Hartley oscillator.
- Or
- (b) With a neat circuit diagram, describe the working of a transistor crystal oscillator.
15. (a) Explain band width and slew rate of an op - amp.

Or

- (b) Discuss the action of inverting amplifier.

Page 4 Code No. : 20034 E
[P.T.O.]

PART C — (5 × 8 = 40 marks)

Answer ALL questions choosing either (a) or (b).
Each answer should not exceed 600 words.

16. (a) State and explain Thevenin's theorem.

Or

- (b) State and explain maximum power transfer theorem.

17. (a) Describe the V – I characteristics of P – N junction diode.

Or

- (b) Discuss the characteristics of a transistor in CE mode.

18. (a) Describe the working characteristics of UJT.

Or

- (b) Explain the operation of push - pull amplifier with circuit.

19. (a) Outline the general theory of feedback.

Or

- (b) What is monostable multivibrator? Explain its working with a neat circuit diagram.

Page 5 Code No. : 20034 E

20. (a) Discuss A.C analysis of OP-AMP.

Or

- (b) Describe the operation of a differential amplifier. Derive an expression for the CMRR.
-

Page 6 Code No. : 20034 E